

数字电子技术（双语） 核心知识点自测题

院(系)_____ 班级_____ 学号_____ 姓名_____

1. (15') Analyze the circuit in Figure1.

- (1) Write the output expression for the circuit.

 


Figure 1

- (2) Develop the truth table for the circuit.

- (3) **Minimize** the gates required to implement the function.

2. (10') A D flip-flop is connected as shown in Figure2. Determine the Q output in relation to the clock and inputs.


 


Figure2

 


3. (20') Implement a three inputs parity checker with odd parity. The output is "1" when the number of input "1" is odd.

(1) Using NAND Gates only


(2) Using a 74LS151 8-inputs data selector/multiplexer.

Function Table of 74LS151



INPUTS			OUTPUT
A ₂	A ₁	A ₀	Y
0	0	0	D ₀
0	0	1	D ₁
0	1	0	D ₂
0	1	1	D ₃
1	0	0	D ₄
1	0	1	D ₅
1	1	0	D ₆
1	1	1	D ₇

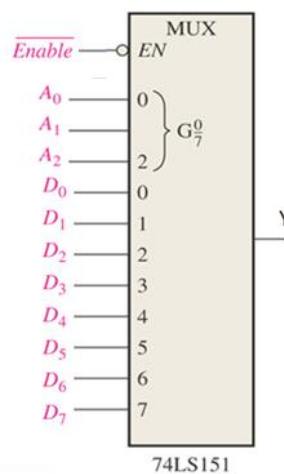

 4. (10') You wish to detect only the presence of the codes 1110, 1001, 0101 and 1011. An active-HIGH output is required to indicate their presence. Develop the logic circuit with a single output that will indicate when any one of these codes is on the inputs. For any other code, the output must be LOW. Please use a 4-line-to-16-line decoder with fewer gates as needed.



  5. (15') Show how to connect two 74LS161s for a modulus-35 counter with sequence $(1, 2, \dots, 35)_{10}$.



6. (15') Determine the sequence of the counter in Figure 3, showing the Q_1 , Q_2 and Q_3 waveforms.


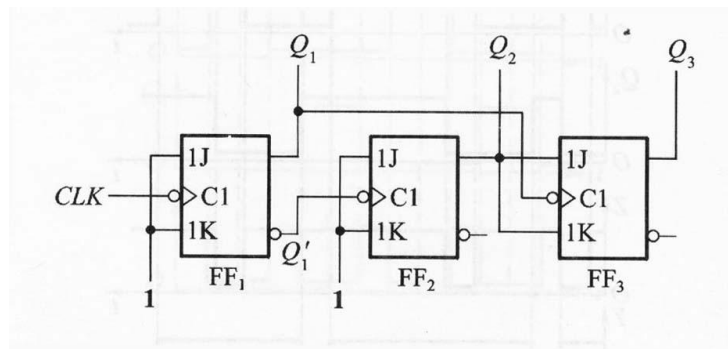


Figure 3

 

7. (15') Design a synchronous counter with sequence $00 \rightarrow 01 \rightarrow 11 \rightarrow 10 \rightarrow 00$, use JK flip-flops.